- PIR motion sensor
 - \circ GND \rightarrow GND
 - HIGH/LOW OUTPUT → D2
 - \circ Power \rightarrow 5 V
- OLED display (I2C)
 - \circ GND \rightarrow GND
 - \circ VCC \rightarrow 5V
 - \circ SCL \rightarrow A5
 - \circ SDA \rightarrow A4
- MicroSD card module
 - \circ 3v3 \rightarrow 3.3 V rail (row)
 - \circ CS \rightarrow L1
 - \circ MOSI \rightarrow L2
 - \circ CLK \rightarrow L3
 - \circ MISO \rightarrow D12
 - \circ GND \rightarrow GND
- DS3231 RTC module
 - \circ SCL \rightarrow A5
 - \circ SDA \rightarrow A4
 - \circ VCC \rightarrow 5V
 - \circ GND \rightarrow GND
- Push button
 - \circ One side \rightarrow GND
 - \circ Other side \rightarrow D7
- Multiple LEDs
 - \circ Red \rightarrow D3
 - \circ Green \rightarrow D4
 - \circ Orange \rightarrow D5
- Passive Buzzer
 - \circ + (Long leg) \rightarrow D6
 - \circ (Short leg) \rightarrow GND
- AMS1117-3.3 DC-DC Step-Down Power
 - \circ Vin \rightarrow 5V
 - Vout \rightarrow 3.3 V Rail (row)
 - \circ GND \rightarrow GND
- 4 Logic Step Down Converter
 - $\circ \quad \mathsf{HV1} \to \mathsf{D10}$
 - \circ HV2 \rightarrow D11

- \circ HV \rightarrow 5.5 V
- $\circ \quad \mathsf{GND} \to \mathsf{GND}$
- \circ HV3 \rightarrow D13
- \circ HV4 \rightarrow
- $\circ \quad \mathsf{LV1} \to \mathsf{CS}$
- \circ LV2 \rightarrow MOSI
- LV \rightarrow 3.3V Rail (row)
- $\circ \quad \mathsf{GND} \to \mathsf{GND}$
- \circ LV3 \rightarrow CLK
- o LV4